

Tribhuvan University
Institute of Science and Technology

2081



Bachelor Level / First Year/ First Semester/ Science

Computer Science and Information Technology (CSC 111)

(Digital Logic)

(OLD COURSE)

Full Marks: 60

Pass Marks: 24

Time: 3 hours.

Candidates are required to give their answers in their own words as far as practicable.
The figures in the margin indicate full marks.

Section A

Attempt any TWO questions.

1. Describe asynchronous counter. Explain binary ripple counter. (2×10=20)
[2+8]
2. Implement $F = \Sigma(0, 2, 3, 5, 6)$ using [4+6]
 - a) Decoder
 - b) PAL
3. Design a combinational circuit that accepts a three bit number and generates an output number equal to the square of the input number. [10]

Section B

Attempt any EIGHT questions.

4. Perform the following conversion (8×5=40)
[2.5+2.5]
 - a) $(145.02)_{10}$ to binary
 - b) $(987)_{16}$ to decimal
5. Design 4 bit even parity generator. [5]
6. How parallel data is converted to serial data and parallel data to serial? Explain with respect to required register. [5]
7. Explain T flip flop. How is it different from SR flip flop? [4+1]
8. Define basic gates, derived gates and universal gates. Illustrate the use of universal gates. [3+2]
9. Simplify the following using k-map where d stands for don't care. [5]

$F(A, B, C, D) = \Sigma(0, 1, 2, 8, 9, 12, 13)$
 $d(A, B, C, D) = \Sigma(10, 11, 14, 15)$
10. Design a half subtractor circuit using only NAND gates. [5]
11. Differentiate between multiplexer and demultiplexer. [5]
12. Write short notes on [2.5+2.5]
 - a) State diagram
 - b) Signed binary number