

Tribhuvan University
Institute of Science and Technology
2081



Bachelor Level / First Year/ First Semester/ Science
Computer Science and Information Technology (CSc. 111)
(Digital Logic)
(OLD COURSE)

Full Marks: 60
Pass Marks: 24
Time: 3 hours.


Candidates are required to give their answers in their own words as far as practicable.
The figures in the margin indicate full marks.

Section A

Attempt any TWO questions.

(2×10=20)

 1. Implement the following function $F = \sum(0,1,3,5,7)$ using
 - a) Decoder
 - b) Multiplexer
 - c) PLA
2. Design clocked sequential circuit of the following state diagram by using RS flip-flop.



3. Implement full adder using Decoder and an OR gate. Explain its working mechanism.

Section B

Attempt any EIGHT questions.

(8×5=40)

4. Represent decimal number 8620 in
 - a) BCD
 - b) Excess-3 code
 - c) 2421 code
 - d) Binary number
5. Express the Boolean function $F = xy + x'z$ in product of maxterm form.

6. Reduce the following function using k-map.
 $F = A'D + BD + B'C + AB'D$
7. Design a combinational circuit that adds one to a 4-bit binary number, $A_3A_2A_1A_0$. For example, if the input of the circuit is $A_3A_2A_1A_0 = 1101$, the output is 1110. The circuit can be designed using four half-adders.
8. Draw a logic diagram of a 2-to-4-line decoder with only NOR gates. Include an enable input.
9. Design the odd parity generator circuit.
10. Draw parallel-in parallel-out shift registers. Explain them.
11. Design a 4-bit binary synchronous counter with D flip-flops.
12. Write short notes on (Any two)
 - a) Reflected code
 - b) CMOS
 - c) Don't care