

Tribhuvan University
Institute of Science and Technology

2077



Bachelor Level / First Year/ First Semester/ Science
Computer Science and Information Technology (CSc. 111)
(Digital Logic)
(NEW COURSE)

Full Marks: 60

Pass Marks: 24

Time: 3 hours.

Candidates are required to give their answers in their own words as far as practicable.

The figures in the margin indicate full marks.

Attempt any two questions:

(2×10=20)


1. Design a combinatorial circuit that generates 9's complement of a BCD number. (10)
2. Implement the following functions using PLA (10)

$$w(A, B, C, D) = \sum(2, 12, 13)$$

$$x(A, B, C, D) = \sum(7, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$y(A, B, C, D) = \sum(0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15)$$
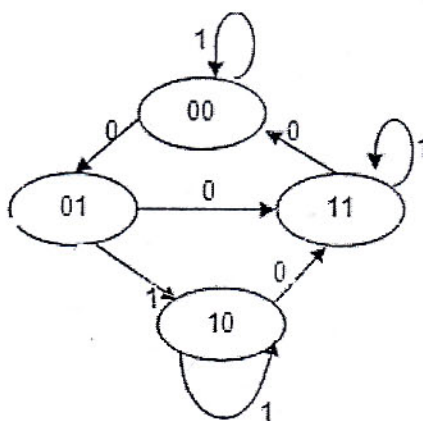
$$z(A, B, C, D) = \sum(1, 2, 8, 12, 13)$$
3. Design sequential circuit specified by the following state diagram using T flip-flops. (10)



4. List two major characteristics of digital computer. Represent -6 (negative six) using 8 bits in signed magnitude, signed-1's-complement and signed-2's-complement respectively. Represent decimal number 4673 in a) octal, and b) BCD. (1+2+2)
5. Where is CMOS suitable to use? Define Power dissipation. Show that the positive logic NAND gate is a negative logic NOR gate and vice versa. (1+1+3)
6. Simplify the following function and implement them with two level NOR gate circuit, $F(w, x, y, z) = wx' + y'z' + w'yz'$ (5)